

**University of Saskatchewan
College of Engineering
EE 341.3: Electrical Machines I
Midterm Examination**

February 13, 2003

Instructor: Dr. N. Kar
Time: 1 hour & 20 min.
Note: Two sheets of handwritten formulas permitted

Marks

- 20 1. (a) The parameters of the equivalent circuit of the 150-kVA, 2,400-V/240-V transformer shown in Fig. 1 are $R_1=0.2 \Omega$, $R_2=0.002 \Omega$, $X_1=0.45 \Omega$, $X_2=0.0045 \Omega$, $R_c=10 \text{ k}\Omega$ and $X_m=1.55 \text{ k}\Omega$. This equivalent circuit is referred to the primary. Determine the
- (a) voltage regulation.
 - (b) efficiency of the transformer operating at rated load with rated voltage of 240 V and 0.8 lagging power factor.

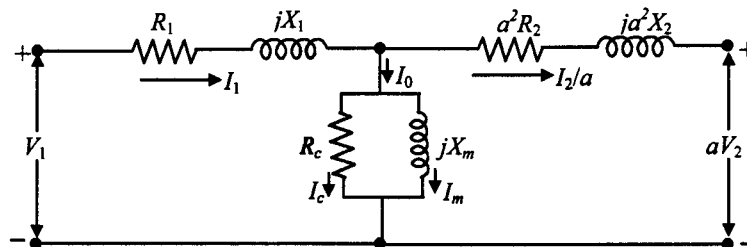


Fig. 1. Transformer equivalent circuit referred to the primary.

- 10 (b) A 3-kVA, 220-V/110-V, 60-Hz, single-phase transformer yields this test data:
- | | |
|---------------------|----------------------|
| open-circuit test: | 200 V, 1.4 A, 50 W |
| short-circuit test: | 4.5 V, 13.64 A, 30 W |
- Determine the efficiency when the transformer delivers a load of 2 kVA at 0.85 power factor lagging.

- 20 2. A three-phase, 220-V, 60-Hz, 4-pole, Y-connected induction motor has a per-phase stator resistance of 0.5Ω . The following no-load and blocked-rotor test data on the motor are given:

No-load test: Line-to-line voltage = 220 V
 Total input power = 600 W, of which 200 W is the friction and windage loss
 Line current = 3 A

Blocked-rotor test: Line-to-line voltage = 35 V
 Total input power = 720 W
 Line current = 15 A

- (a) Calculate the parameters of the equivalent circuit shown in Fig. 2.
 (b) Find the output power, output torque, and efficiency if the machine runs as a motor with a slip of 0.05.

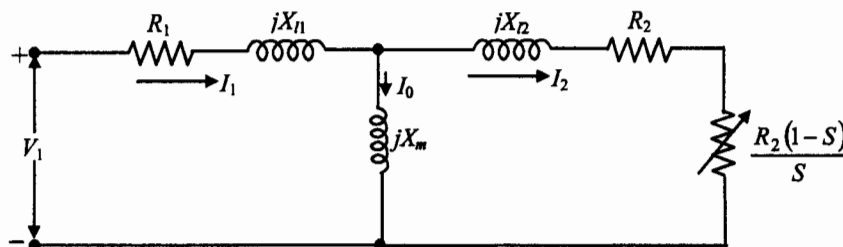


Fig. 2. Induction motor equivalent circuit referred to the stator.

———— THE END ————