

**University of Saskatchewan  
EE 341.3 Electric Machines I  
Mid-Term Examination**

**Dated: March 3, 2008**  
**Instructor: Dr. Rama Gokaraju**

**Time: 6:00pm-8:00pm**  
**Total Marks: 30**

---

**Problem 1**

The parameters of a 12 kVA, 120/360 V, 60 Hz, two-winding, step-up transformer are  $R_H=0.6 \Omega$ ,  $X_H= 1.2 \Omega$ ,  $R_L=0.1 \Omega$ ,  $X_L= 0.3\Omega$ ,  $R_{c,H}=3.2 \text{ k}\Omega$  (found from high-voltage side) and  $X_{m,H}=25 \text{ k}\Omega$  (found from high-voltage side).

The two-winding transformer is connected as a 120/480 V, step-up autotransformer. It delivers its rated load at 0.8 pf lagging. Determine its efficiency.

**10 Marks**

**Problem 2**

A three-phase generator is connected to a three-phase load via a 220/2200 V,  $\Delta$ -Y connected, three-phase, step-up transformer, a short transmission line, and a 2200/220 V, Y-  $\Delta$  connected step-down transformer. The per-phase winding resistance and the leakage reactance as referred to the high-voltage side for each transformer are  $1.2 \Omega$  and  $4.8 \Omega$ , respectively. Neglect the core-loss resistance and the magnetizing reactance of the transformers. The impedance of the transmission line is  $2.5 + j2.1 \Omega$ . The per-phase reactance of the generator is  $j1.2 \Omega$  (neglect the per-phase winding resistance of the generator). If the load is 50 kVA at 220 V and a lagging pf of 0.8, determine the generator voltage. Use the pu system for calculations.

**10 Marks**

**Problem 3**

The following readings are taken from the results of open-circuit and short-circuit tests on a 10 MVA, three-phase, Y-connected, 13.8 kV, 2-pole, 60 Hz synchronous generator driven at synchronous speed:

Field current, A:	170	200
Armature current, short-circuit test, A:	418	460
Line-to-line voltage, open-circuit test, V:	13,000	13,800
Line-to-line voltage, air-gap line, V	15,500	17,500

Neglect the armature resistance.

- a) Determine the unsaturated value of the synchronous reactance in ohms per phase.
- b) Compute the saturated value of the synchronous reactance in ohms per phase.
- c) Find the short-circuit ratio.

**5 Marks**

#### **Problem 4**

A three-phase, Y-connected, 2300 V, 60 Hz round-rotor synchronous generator has a synchronous reactance of  $2 \Omega$  per phase and negligible armature resistance.

- a) If the generator supplies a line current of 350 A operating at 0.8 pf leading, calculate the excitation voltage and the power angle.
- b) If the generator is operating on load with a power angle of  $20^\circ$ , and the excitation is adjusted so that the excitation voltage is equal in magnitude to the terminal voltage, determine the armature current and the power factor of the generator.

**5 Marks**

---