

EE 391 (All Sections)

Midterm Examination

Tuesday, October 31, 2006

Time Allowed: 2 Hours

Materials allowed: Laboratory Notebooks, Calculators

Instructions:

- Answer all questions in the space provided (use page backs for rough work if necessary)
- State your assumptions; show all relevant work. Box, circle or otherwise highlight your answers where appropriate. For multiple choice, circle the correct answer.
- *Put your name and student number on each page; (we may separate them for marking purposes)*
- Refer to the last page for relevant product data when required
- Weighting for each question is indicated in the left margin (Total marks: 120)

(Marker's use only.)

S. L.	Noise	Op A	Fourier	2 nd Ord	FET	Total
15 /20	/21	/19	/20	/20	/20	85 /120


Name: Craig Bloch-Hansen

Student Number: 10147742

Timing in Sequential Logic

Q1.1) In general, a ring of N inverters with an average propagation delay of t_p , will oscillate with a frequency of $\frac{1}{2Nt_p}$ and a period of $2Nt_p$. N must be odd (circle one) number of inverters.

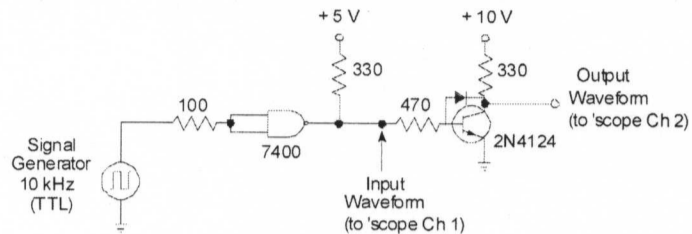
Q1.2) Consider the basic inverter circuit shown below driven by a 10kHz TTL square wave from the signal generator.



The oscilloscope trace of the input and output waveforms are shown at right. Determine the values of the following parameters *if shown*, and label them on the 'scope figure.

[6]

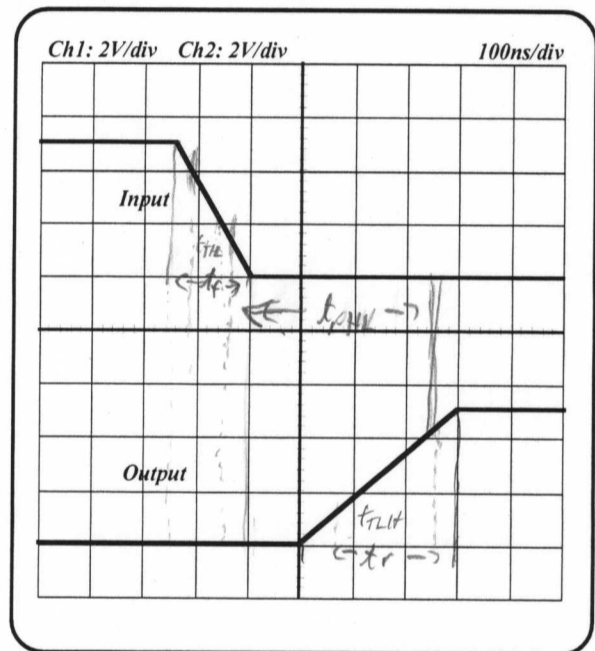- i) t_r ~~300 ns~~
- ii) t_f ~~150 ns~~
- iii) t_{PLH} ~~400 ns~~
- iv) t_{PHL} Not shown
- v) t_{THL} ~~50 ns~~
- vi) t_{TLH} ~~200 ns~~



4

