

**UNIVERSITY OF SASKATCHEWAN  
MIDTERM EXAMINATION**

**EE 486.3/402.3      Microwave Engineering**

Professor:    Dr. D. M. Klymyshyn

February 28, 2002


Time:        **80 minutes**

Notes:      One formula sheet is allowed.  
               2-port parameter conversion sheet is allowed.  
               All 3 questions are of equal value.  
               Assume all transmission lines are lossless.

1.    A microwave circuit is shown. The power **available** from the source ( $P_{avs}$ ) is 0 dBm. Using **transmission line equations** (not the Smith Chart), find the following:


a.     $|V|$  at points  $A$ ,  $B$ , and  $L$ .

b.    Average power at points  $A$ ,  $B$ , and  $L$  using  $\frac{1}{2} \frac{|V(-l)|^2}{|Z(-l)|} \text{Re}(Z(-l))$ .

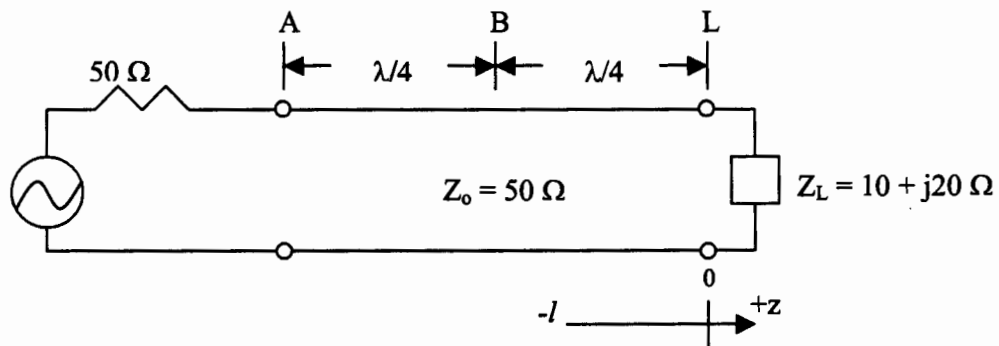

2. The [S] parameters of the amplifier **alone** as measured in a  $50\ \Omega$  system are given. A resistor is added to the amplifier as shown. Does this **increase** or **decrease** the **power gain** (note: **not** voltage gain) of the overall 2-port network and by how much?

(HINTS: The power gain of a 2-port network with source and load terminated in  $Z_o$  is  $20 \log |S_{21}|$ . [Y] parameters of the amplifier **alone** are also given.)

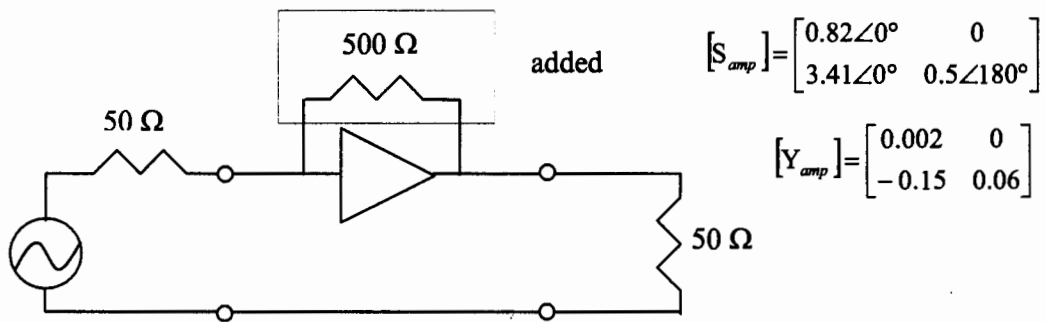

$$[S_{amp}] = \begin{bmatrix} 0.82 \angle 0^\circ & 0 \\ 3.41 \angle 0^\circ & 0.5 \angle 180^\circ \end{bmatrix}$$

$$[Y_{amp}] = \begin{bmatrix} 0.002 & 0 \\ -0.15 & 0.06 \end{bmatrix}$$

3. Design an **open circuit single shunt** stub tuner to match a  $100\ \Omega$  load to a  $50\ \Omega$  line. The stub should be as **close as possible** to the load. Use  $50\ \Omega$  transmission lines for the tuner. Include the **Smith Chart** provided with your solution, **clearly** marking all constructions.