

EE431 Quiz No. 3: Written

Date: Thursday, November 29, 2001

Time = 40 minutes

Texts and Notes allowed

1. Generate a schematic diagram for the Verilog descriptions given below. For the flip/flops in your schematic, use a D type with clock enable, asynchronous set and asynchronous clear.

- (1) (a) module circuit_1 (clk, a, b, c, Q)
input clk, a, b, c;
output Q;
reg Q;
always @ (posedge clk)
begin
if (a == 1'b1) Q <= 1'b1
else if (b == 1'b1) Q <= c;
else Q <= c ^ Q;
end
- (1) (b) module circuit_2 (clk, a, b, c, d, r)
input clk, a, b, r;
input [1:0] c;
output d;
reg Q1, Q2, d;
always @ (posedge clk or negedge r)
if (r == 1'b0) begin Q1 <= 1'b0; Q2 <= 1'b0; end
else
if (a == b)
case (c)
2'b00: begin Q1 <= c[1]; Q2 <= Q1; end
2'b01: begin Q1 <= d ^ Q2; Q2 <= b; end
2'b10: begin Q1 <= d; Q2 <= Q1; end
2'b11: begin Q1 <= d; Q2 <= Q1; end
endcase
else begin Q1 <= 1'b0; Q2 <= 1'b1; end

```
always @ (Q1 or Q2 or d)
if (a == Q2) d = Q1;
else if (Q1 == Q2) d = Q2;
else d = b;
```

```
endmodule
```

2. Consider the structural description below

```
module circuit_3(clk, y)
input clk;
output y
wire x, d;
DFFE flop_1 (.clk(clk), .d(d), .Q(x));
DFFE flop_2 (.clk(clk), .d(x), .Q(y));
nor nor_1(d,x,y);
endmodule
```

DESCRIPTION OF CONNECTION LIST FOR D FLOP

```
DFFE instance_name (
.D(d),          // the d input
.CLK(clk),     // the clock, positive edge trigger
.ENA(enable),  // if used, D goes to Q on clock edge when
               // ENA is high otherwise Q does not change
.CLRN(clear_bar), // if used, clears Q when low
.PRN(set_bar),   // if used, sets Q when low
.Q(q)          // output
);
```

- (1) (a) Write a behavioral description in Verilog of the circuit described above. For this description use only blocking equalities in the "always" constructs.

- (1) (b) Write a behavioral description in Verilog of the circuit described above. For this description use only non-blocking equalities in the "always" constructs.

3. Consider the structural description below

```
module circuit_4(clk_1, clk_2, y)
input clk_1, clk_2;
output y
wire x, w;
DFFE flop_1 (.CLK(clk_1), .D(1'b1), .CLR(y), .Q(x));
DFFE flop_2 (.CLK(clk_2), .D(1'b1), .CLR(y), .Q(w));
nand nand_1 (y,w,x);
endmodule
```

- (1) (a) Write a behavioral description in Verilog of the circuit described above. For this description use only blocking equalities in the "always" constructs.
- (1) (b) Write a behavioral description in Verilog of the circuit described above. For this description use only non-blocking equalities in the "always" constructs.