

3.

The [S] parameters of a **potentially unstable** transistor measured in a 50Ω system are given. Evaluate the **load stability** of the transistor; a Smith Chart is included for your solution. Is the termination $\Gamma_L = 0.9 \angle -80^\circ$ a good choice for load termination? Explain.

$$[S_{trans}] = \begin{bmatrix} 0.75 \angle 160^\circ & 0.1 \angle 20^\circ \\ 8.2 \angle 50^\circ & 0.25 \angle 0^\circ \end{bmatrix}$$

4.

The [S] parameters for a transistor as measured in a 50Ω system are given. Find **real** valued source and load terminations to give a transducer power gain $G_T = 10$ dB. Use the attached Smith Chart for your solution. You do not need to design the matching circuits.

$$[S_{trans}] = \begin{bmatrix} 0.72 \angle 20^\circ & 0 \\ 2.51 \angle 100^\circ & 0 \end{bmatrix}$$



UNIVERSITY OF SASKATCHEWAN EXAMINATION BOOKLET

PLEASE PRINT CLEARLY

SURNAME NESS
FIRSTNAME KYLE

STUDENT NUMBER

9 6 1 0 1 6

CLASS (e.g. BIOL 110 02)

E E
SUBJECT

4 5 8
COURSE NUMBER

0 2
SECTION NUMBER

BOOKLET NUMBER 1

TOTAL NUMBER OF BOOKLETS HANDED IN 1

I declare that I am the person named. I am formally registered as a student in the class indicated on this cover page.

SIGNATURE Kyle Ness

DATE March 1, 2005

INSTRUCTIONS TO CANDIDATES

- Cheating on an examination is considered a serious offence by the University and can be met with disciplinary action, including suspension or expulsion.
- Candidates shall not bring into the examination room any books, resources or papers except at the discretion of the examiner or as indicated on the examination paper.
- Students are required to have suitable identification (student I.D. card or other picture I.D.) available during examinations. Invigilators may request that students produce such identification during examinations.
- Candidates shall hold no communication of any kind with other candidates within the examination room.
- If you require information concerning the question paper, hold up your hand. If you require paper, hold up an examination booklet.
- Unless permission has been granted by the invigilator, candidates may leave their seats only to turn in their answer booklets.
- Before leaving the examination room, all students are required to sign a tally sheet indicating their attendance at the final examination and submission of examination materials.
- The number of booklets used must be indicated on the tally sheet. If more than one booklet is used, ensure that all additional booklets are properly marked and placed inside the first booklet. All booklets supplied must be returned to the invigilator.

MARKER'S USE ONLY

- 8
- 5
- 10
- 7
- _____
- _____
- _____
- _____
- _____
- _____
- _____
- _____


30

TOTAL


①

8

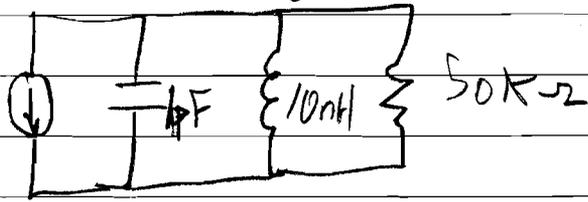$Q_{ind} = 46 \text{ at } 100 \text{ MHz}$


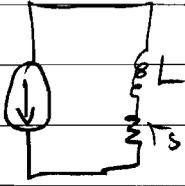
$$Q_{ind_{new}} = \frac{(10 \times 10^9 \frac{\text{rad}}{\text{s}})(10 \times 10^{-9} \text{H})}{0.137 \Omega} = 729.93$$




$$Q_{ind} = \frac{\omega_0 L}{r_s}$$

$$r_s = \frac{\omega_0 L}{Q_{ind}} = \frac{2\pi(100 \times 10^6)(10 \times 10^{-9} \text{H})}{46}$$

$$r_s = 0.137 \Omega$$

~~$$R_p = (Q_{ind})^2 r_s = (46)^2 (0.137 \Omega) = 289 \Omega$$~~
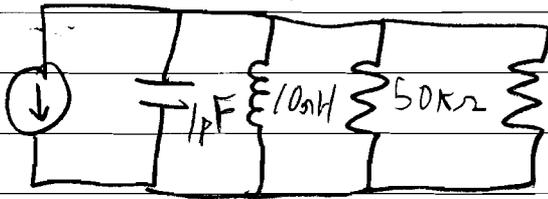
$$R_p = (Q_{ind_{new}})^2 r_s = (729.93)^2 (0.137 \Omega) = 73 \text{ k}\Omega$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1 \times 10^{-12} \text{F})(10 \times 10^{-9} \text{H})}} = 10 \times 10^9 \frac{\text{rad}}{\text{s}}$$

~~$$Q = \frac{R_p \parallel 50 \text{ k}\Omega}{\omega_0 L} = \frac{(289 \Omega) \parallel (50 \times 10^3 \Omega)}{289 \Omega + 50 \times 10^3 \Omega} = \frac{(10 \times 10^9 \frac{\text{rad}}{\text{s}})(10 \times 10^{-9} \text{H})}{289 \Omega + 50 \times 10^3 \Omega}$$~~


Q = 2.87

$$Q = \frac{R_p \parallel 50 \text{ k}\Omega}{\omega_0 L} = \frac{(73 \times 10^3 \Omega) \parallel (50 \times 10^3 \Omega)}{73 \times 10^3 \Omega + 50 \times 10^3 \Omega} = \frac{(10 \times 10^9 \frac{\text{rad}}{\text{s}})(10 \times 10^{-9} \text{H})}{73 \times 10^3 \Omega + 50 \times 10^3 \Omega}$$

Q = 297

② $P_{AVN} = 500 \text{ mW}$ $\Gamma_L = 0.5 \angle 90^\circ$
 $Z_0 = 50 \Omega$ ~~P_{AVS}~~

Find G_T

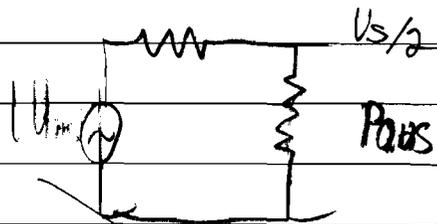

$$P_{AVS} = \frac{|U_s|^2}{8Z_0}$$

$$= \frac{(1 \text{ V})^2}{8(50 \Omega)} = 2.5 \text{ mW}$$

$$P_{AVS} = \frac{|U_s|^2}{4Z_0} = \frac{(1 \text{ V}_{rms})^2}{4(50 \Omega)}$$

$$P_{AVS} = 5 \text{ mW}$$

~~$$P_{AVS} = \frac{(1 \text{ V}_{rms})^2}{8Z_0} = \frac{(1 \text{ V})^2}{8(50 \Omega)}$$~~

NO since $Z_L \neq Z_{out}$

Need P_L since $G_T = \frac{P_L}{P_{AVS}}$

~~$$P_L = P_{AVN} (1 - |\Gamma_L|^2) = 500 \text{ mW} (1 - |0.5|^2) = 375 \text{ mW}$$~~

~~$$G_T = \frac{375 \text{ mW}}{2.5 \text{ mW}} = 150 \text{ (21.76 dB)}$$~~

Since we have some power reflected off the load b/c Γ_L is not 0 meaning no reflection we get $P_L < P_{AVN}$ and can then find G_T .

~~$$\Gamma_{out} = 0.5 \angle -90^\circ = -j0.5$$~~

~~$$P_L = P_{AVN} M_L$$~~

~~$$M_L = \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_{out}|^2)}{|1 - \Gamma_L \Gamma_{out}|^2} = \frac{(1 - 0.25)(1 - 0.25)}{|1 - (-j0.5)(j0.5)|^2} = 0.692$$~~

~~$$G_T = \frac{P_L}{P_{AVS}} = \frac{P_{AVN} M_L}{P_{AVS}} = 69.2 \text{ (18.4 dB)}$$~~

③ Evaluate Stability

10

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

$$\Delta = (0.75 \angle 160^\circ)(0.25 \angle 0^\circ) - (0.1 \angle 20^\circ)(8.2 \angle 50^\circ)$$

$$\Delta = 0.841 \angle -123^\circ$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{21} S_{12}|}$$

$$K = \frac{1 - (0.75)^2 - (0.25)^2 + (0.841)^2}{2|(0.1 \angle 20^\circ)(8.2 \angle 50^\circ)|}$$

$$K = 0.66$$

Since $K < 1$ & $|\Delta| > 1$ we have potentially unstable systems as stated in question.

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = \frac{0.25 \angle 0^\circ - [(0.841 \angle -123^\circ)(0.75 \angle 160^\circ)]^*}{(0.25)^2 - (0.841)^2}$$

$$C_L = 0.968 \angle -100^\circ$$

$$\Gamma_L = \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} = \frac{(0.1 \angle 20^\circ)(8.2 \angle 50^\circ)}{(0.25)^2 - (0.841)^2}$$

$$\Gamma_L = 1.27$$

Since $|S_{11}| < 1$ then $\Gamma_L = 0$ corresponds to the center of the smith chart and $|\Gamma_{in}| = |S_{11}|$ so.

Yes $\Gamma_L = 0.9 \angle -80^\circ$ is a good choice because when $\Gamma_L = 0$ $|\Gamma_{in}| = |S_{11}|$ and so $|\Gamma_{in}| < 1$ inside the circle drawn on the smith chart and so load is stable here and when $\Gamma_L = 0.9 \angle -80^\circ$ it falls inside this circle.

④

$$K = S_{11}S_{22} - S_{12}S_{21}$$

$$\Delta = (0.72 \angle 200^\circ)(0) - (0)(2.51 \angle 100^\circ)$$

$$\Delta = 0 \angle 0^\circ$$

Unilateral Case

$$G_0 = |S_{21}|^2 = (2.51)^2 = 6.3 \quad (7.99 \text{ dB})$$

$$G_{S \max} = \frac{1}{1 - |S_{11}|^2} = \frac{1}{1 - (0.72)^2} = 2.076 \quad (3.17 \text{ dB})$$

$$G_{L \max} = \frac{1}{1 - |S_{22}|^2} = 1 \quad (0 \text{ dB})$$

No gain can be retrieved from the load but you can get some from the source.

To get $G_T = 10$ we need $G_S = 10 - 7.99 = 2 \text{ dB}$

$$g_{2 \text{ dB}} = \frac{2 \text{ dB}}{3.17 \text{ dB}} = 0.631$$

$$C_{gi} = \frac{g_{2 \text{ dB}} S_{11}^*}{1 - |S_{11}|^2 (1 - g_{2 \text{ dB}})} = \frac{0.631 (0.72 \angle -200^\circ)}{1 - (0.72)^2 (1 - 0.631)}$$

$$C_{gi} = \frac{0.567 \angle -200^\circ}{\sqrt{1 - g_{2 \text{ dB}} (1 - |S_{11}|^2)}}$$

$$\Gamma_{g_{2 \text{ dB}}} = \frac{1 - |S_{11}|^2 (1 - g_{2 \text{ dB}})}{1 - (0.72)^2 (1 - 0.631)}$$

$$\Gamma_{g_{2 \text{ dB}}} = 0.362$$

Resistive load termination of either:

$$(2)(50) = \boxed{600 \Omega}$$

OR

$$(1.55)(50 \Omega) = \boxed{77.5 \Omega}$$

will yield $G_T = 10 \text{ dB}$.

For the load

$$g_i = 0 \text{ dB}$$

$$C_{0 \text{ dB}} = 0$$

$$\Gamma_{g_i} = \frac{\sqrt{1-0} (1-|S_{22}|^2)}{1-|S_{22}|^2 (1-0)} = \frac{1(1-0)}{1-0} = \underline{\underline{1}}$$

X
/ Any where on the edge of the Smith chart will make the load gain = 0 dB so for real values either a short or an open at the load termination will yield a gain of 0 dB using a purely real load termination.

SOP

$$g_{0 \text{ dB}} = \frac{\left(\frac{2 \text{ dB}}{10}\right)}{\frac{10 \left(\frac{3.17289}{10}\right)}{10}} = \frac{1.58}{2.07} = \underline{\underline{0.7638}}$$

$$C_{g_i} = \frac{0.7638 (0.77 \angle -70^\circ)}{1 - (0.77)^2 (1 - 0.7638)} = \underline{\underline{0.626 \angle -70^\circ}}$$

$$\Gamma_g = \frac{\sqrt{1-0} \sqrt{1-0.7638} (1-0.77)}{1 - (0.77)^2 (1-0.7638)} = \underline{\underline{0.26 \angle -70^\circ}}$$

Source termination of

$$Z_S = 125 \Omega \text{ or } 350 \Omega$$

$$Z_L = 50 \Omega$$