

Engineering Physics 214 Midterm

There are five questions worth a total of 44 marks
No calculators or notes are allowed, a formula sheet is provided.
Question parts are equally weighted unless otherwise specified.

Tuesday March 3rd, 2015

- (8 marks) Answer the following questions assuming $z_1 = -1 + j\sqrt{3}$ and $z_2 = \sqrt{2}e^{j\frac{\pi}{4}}$.
 - Express z_1 in the form of $Me^{j\phi}$
 - Express z_2 in the form of $x + jy$
 - What is z_1z_2 ?
 - What is $\frac{z_1}{z_2}$?
 - At what frequency does e^{z_1t} oscillate?
- (4 marks) Derive (through integration) the Laplace transform of:
$$f(t) = \sin(at),$$
assuming $f(t)$ begins at time $t = 0$.
- (12 marks) Consider the series RLC circuit shown in Figure 1 with arbitrary input voltage and a switch that closes at $t = 0$.

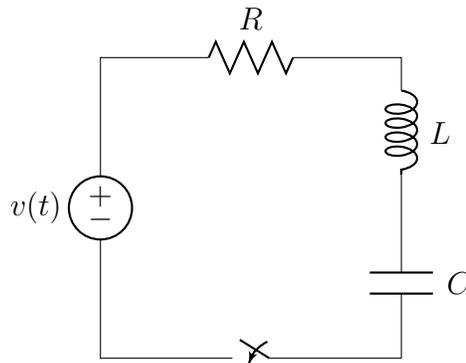


Figure 1: RLC circuit.

- What is the differential equation that describes the current in the circuit?
- Derive the transfer function for the current.
- Derive the unit impulse response for the current assuming the system is critically damped.
- If the circuit is driven by a voltage $v(t) = \tilde{A}e^{j\omega t}$ what is the Laplace transform of the current, $I(s)$, assuming all initial conditions are zero?

4. (14 marks) Consider the series RC circuit shown in Figure 2 where the switch closes at $t = 0$.

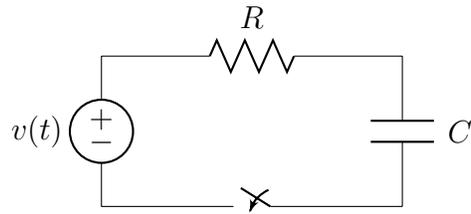


Figure 2: RC circuit.

- (a) (4 marks) Derive the zero input response of the capacitor voltage assuming an initial charge of $q(0) = q_0$.
- (b) (4 marks) Derive the transfer function for the voltage across the capacitor.
- (c) (4 marks) If the circuit is driven by a constant voltage, $v(t) = V_0$, derive the capacitor voltage as a function of time.
- (d) (2 marks) If the circuit is driven by the voltage, $v(t) = \frac{1}{t} \sin(\omega t)u(t)$, what is the capacitor voltage as a function of time. State your answer in the form of an integral but do not evaluate it.
5. (6 marks) Consider a damped mass-spring system described by the equation


$$m\ddot{x} + b\dot{x} + kx = 0.$$

Where $k = 2 \text{ N/m}$ and $m = 8 \text{ kg}$.

- (a) What is the damping factor, b , that results in a critically damped system?
- (b) If the system is underdamped sketch the position of the mass as a function of time if $\dot{x}(0) = 0 \text{ m/s}$ and $x(0) = 1 \text{ m}$. On this same plot sketch an example of a critically damped case with the same initial conditions.

End of Exam

$$1) z_1 = -1 + j\sqrt{3}$$

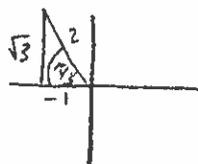

$$z_1 = 2e^{j2\pi/3}$$

$$b) z_2 = \sqrt{2}e^{j\pi/4}$$



$$z_2 = 1 + j$$

$$\begin{aligned} c) z_1 z_2 &= M_1 M_2 e^{j(\phi_1 + \phi_2)} \\ &= 2\sqrt{2} e^{j(2\pi/3 + \pi/4)} \\ &= 2\sqrt{2} e^{j(11\pi/12)} \end{aligned}$$

$$\begin{aligned} d) z_1/z_2 &= M_1/M_2 e^{j(\phi_1 - \phi_2)} \\ &= 2/\sqrt{2} e^{j(2\pi/3 - \pi/4)} \\ &= \sqrt{2} e^{j(5\pi/12)} \end{aligned}$$

$$e) e^{z_1 t} = e^{t(-1 + j\sqrt{3})} = e^{-t} e^{j\sqrt{3}t} = e^{-t} (\cos(\sqrt{3}t) + j\sin(\sqrt{3}t))$$

$$\omega = \sqrt{3} \rightarrow f = \sqrt{3}/2\pi$$

$$\begin{aligned} 2) F(s) &= \int_0^{\infty} \sin(at) e^{-st} dt = \frac{1}{2j} \int_0^{\infty} (e^{jat} - e^{-jat}) e^{-st} dt \\ &= \frac{1}{2j} \int_0^{\infty} (e^{(-s+ja)t} - e^{(-s-ja)t}) dt \\ &= \frac{1}{2j} \left[\frac{1}{-s+ja} e^{(-s+ja)t} - \frac{1}{-s-ja} e^{(-s-ja)t} \right]_0^{\infty} \\ &= \frac{1}{2j} \left[\frac{1}{-s+ja} (0-1) - \frac{1}{-s-ja} (0-1) \right] \\ &= \frac{1}{2j} \left[\frac{1}{-s-ja} - \frac{1}{-s+ja} \right] \\ &= \frac{1}{2j} \left[\frac{-s+ja + s+ja}{(-s-ja)(-s+ja)} \right] = \frac{1}{2j} \frac{2ja}{s^2 + a^2} \\ &= \frac{a}{s^2 + a^2} \end{aligned}$$

$$3a) \quad v_L + v_C + v_R = v$$

$$\frac{di}{dt}L + \frac{1}{C} \int_0^t i(\tau) d\tau + \frac{q_0}{C} + iR = v$$

$$b) \quad sI(s)L + \frac{1}{sC}I(s) + \frac{q_0}{sC} + I(s)R = V(s)$$

$q_0 = 0$

$$I(s) \left(sL + R + \frac{1}{sC} \right) = V(s)$$

$$H(s) = \frac{I(s)}{V(s)} = \frac{1}{sL + R + \frac{1}{sC}} = \frac{s}{s^2L + sR + \frac{1}{C}}$$

$$c) \quad h(t) = \mathcal{L}^{-1}(H(s))$$

$$H(s) = \frac{s/L}{(s-s_1)(s-s_2)} = \frac{A}{s-s_1} + \frac{B}{(s-s_1)^2}$$

Since $s_1 = s_2$
we have a
double root

OR

$$h(t) = \frac{1}{L} \frac{d}{dt} (t e^{s_1 t})$$

↑ from multiplication by s in the frequency domain

$$h(t) = \frac{1}{L} (s_1 t e^{s_1 t} + e^{s_1 t})$$

$$d) \quad v(t) = \tilde{A} e^{j\omega t} \rightarrow V(s) = \frac{\tilde{A}}{s - j\omega}$$

$$I(s) = H(s)V(s) = \frac{\tilde{A}}{s - j\omega} \frac{s}{(s-s_1)^2} \cdot \frac{1}{L}$$

$$4 \ a) \quad v = v_R + v_C$$

$$v = \dot{q}R + q/C$$

$$V = sQR - q(0)R + Q/C$$

$$V = Q(sR + 1/C) - q_0 R \quad \text{Zero input when } V=0$$

$$Q(s) = \frac{q_0 R}{sR + 1/C}$$

$$= q_0 R \left(\frac{1}{sR + 1/C} \right) = q_0 R \left(\frac{1/R}{s + 1/RC} \right)$$

$$q(t) = q_0 e^{-t/RC} \rightarrow v_C(t) = \frac{q_0}{C} e^{-t/RC}$$

$$b) \quad V(s) = Q(s) (sR + 1/C)$$

$$\frac{Q(s)}{V(s)} = \frac{1}{sR + 1/C} = \frac{1}{R} \frac{1}{s + 1/RC}$$

$$H_Q(s) = \frac{1}{R} \frac{1}{s + 1/RC} \rightarrow H_{V_C} = \frac{1}{RC} \frac{1}{s + 1/RC}$$

$$c) \quad v(t) = V_0 \rightarrow V(s) = \frac{V_0}{s}$$

$$V_C(s) = V(s) H_{V_C}(s) = \frac{V_0}{RCs} \frac{1}{s + 1/RC}$$

$$v_C(t) = \frac{1}{s_1 - s_2} (e^{s_1 t} - e^{s_2 t}) = \frac{V_0}{RC} RC (e^{0t} - e^{-t/RC})$$

$$= V_0 (1 - e^{-t/RC}) + \frac{q_0}{C} e^{-t/RC}$$

$$d) \quad v_C(t) = h(t) * v(t) + ZIR$$

$$= \underbrace{\int_0^t \frac{1}{t} \sin(\omega t) \frac{1}{RC} e^{-t/RC} dt}_{ZSR} + \underbrace{q_0 e^{-t/RC}/C}_{ZIR}$$

5) a) let $\alpha = \frac{b}{2m}$ $\omega_0 = \sqrt{\frac{k}{m}}$

$$\frac{b}{2m} = \sqrt{\frac{k}{m}} \rightarrow b = 2m\sqrt{\frac{k}{m}} = 2\sqrt{km}$$

$$b = 2\sqrt{2 \cdot 8} = 8 \text{ kg/s}$$

