

EP 214 - 2016 Midterm - Question 1 Solution

a) $z(t) = 3.2 e^{-j(\omega t + \theta)}$

$\omega = 2\pi f$
 $f = 100 \text{ Hz}$
 $\theta = \pi/7$
 $t = 2 \text{ ms}$

$\omega = 200\pi \text{ rad/s}$

$\omega t = (200\pi)(0.002) = 0.4\pi$

$\omega t + \theta = 1.7054$

$z(t) = 3.2 e^{-j1.7054}$

← not between zero and 2π

$z(t) = 3.2 e^{j4.58}$

↖ θ between $[0, 2\pi]$.

b) $\dot{z}(t) = -j\omega 3.2 e^{-j(\omega t + \theta)}$

$\theta = \pi/2$ $\omega t = \pi/2$

$f = 100 \text{ Hz}$
 $t = 0.0025 \text{ s}$
 $\theta = \pi/2$

$\omega = 200\pi$

$\dot{z}(t) = -j(200\pi)(3.2) e^{-j\pi}$

$= 640\pi j = \boxed{640\pi e^{j\pi/2} = \dot{z}(t)}$

Question 1

②

c)

$$Z(\omega) = \frac{Z_C}{Z_C + Z_R}$$

$$Z_R = R = 10\Omega$$
$$Z_C = \frac{-j}{\omega C} = -j10\Omega$$

$$\omega = 1 \times 10^5 \frac{\text{rad}}{\text{s}}$$

$$C = 1\mu\text{F}$$

$$Z(\omega) = \frac{-j10\Omega}{10\Omega - j10\Omega} = \frac{10}{10} \left(\frac{-j}{1-j} \right) = \frac{-j(1+j)}{2}$$

$$Z(\omega) = \frac{1-j}{2} = 0.7071 e^{j5.4978}$$

Question 2 solutions

(1)

a)
$$\ddot{q} + 2\alpha \dot{q} + \beta q = \frac{v(t)}{L}$$

$$\alpha = \frac{R}{2L} \quad \beta = \frac{1}{LC}$$

b) Use

$$L \frac{di}{dt} + iR + \frac{q(0)}{C} + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

$$LsI(s) + I(s)R + \frac{q(0)}{C} \frac{1}{s} + \frac{I(s)}{sC} = V(s)$$

$$I(s) [Ls + R + \frac{1}{sC}] = V(s) - \frac{q(0)}{C} \frac{1}{s}$$

OR
$$\frac{sV(s)}{L} \frac{1}{s^2 + 2\alpha s + \beta} - \frac{\beta q(0)}{s^2 + 2\alpha s + \beta}$$

$$I(s) = \frac{V(s)}{sL + R + \frac{1}{sC}} - \frac{q(0)}{C} \frac{1}{s} \frac{1}{sL + R + \frac{1}{sC}}$$

c) Use
$$\ddot{q} + 2\alpha \dot{q} + \beta q = \frac{v(t)}{L}$$

$q(0) = 0$
as we
are looking
for
unit impulse
response.

$$s^2 Q(s) + 2\alpha s Q(s) + \beta Q(s) = \frac{V(s)}{L}$$

but $V(s) = 1$



Question 2 Solutions

2

so

$$Q(s) = H(s) = \frac{1}{L} \frac{1}{s^2 + 2\alpha s + \beta}$$
$$= \frac{1}{L} \frac{1}{(s-s_1)} \frac{1}{(s-s_2)}$$

so

$$h(t) = \frac{1}{L} \frac{1}{(s_1 - s_2)} [e^{s_1 t} - e^{s_2 t}]$$

from tables of transforms

d) For no initial conditions.

$$I(s) = \frac{V(s)}{sL + R + 1/sC}$$

for Transfer functions $V(s) = 1$

$$H_I(s) = \frac{1}{sL + R + 1/sC}$$

since $V_L(s) = sLI(s)$ for zero initial conditions

3

$$V_L(s) = sL \frac{V(s)}{sL + R + 1/sC}$$

and
$$H_{V_L}(s) = \frac{sL}{sL + R + 1/sC}$$

e) Use $\ddot{q} + 2\alpha\dot{q} + \beta q = \frac{v(t)}{L}$

but $q(0) \neq 0$ and $\dot{q}(0) = 0$

so
$$\frac{V(s)}{L} = s^2 Q(s) - sq(0) + 2\alpha[sQ(s) - \dot{q}(0)] + \beta Q(s)$$

with $V(s) = A \frac{s}{\omega^2 + s^2}$.

so
$$Q(s) = \frac{V(s)}{L(s^2 + 2\alpha s + \beta)} + \frac{sq(0) + 2\alpha\dot{q}(0)}{(s^2 + 2\alpha s + \beta)}$$

$$Q(s) = \frac{A}{L} \frac{s}{\omega^2 + s^2} \frac{1}{(s^2 + 2\alpha s + \beta)} + \frac{sq(0) + 2\alpha\dot{q}(0)}{(s^2 + 2\alpha s + \beta)}$$

Question 3

①

$$a) \quad L \frac{di}{dt} + iR = v(t)$$

$$b) \quad i(0) = 0 \quad sL I(s) + RI(s) = 1$$

transfer function

$$I(s) = \frac{1}{R + sL} = H(s)$$

$$c) \quad H(s) = \frac{1}{L} \frac{1}{s + R/L} \quad \text{so} \quad h(t) = \frac{1}{L} e^{-R/L t}$$

$$d) \quad i(t) = h(t) * v(t)$$

$$i(t) = \int_0^{\infty} v(t-z) \frac{1}{L} e^{-R/L z} dz$$

$$e) \quad I(s) = \frac{V(s)}{R + sL} \quad V(s) = \frac{\tilde{A}}{s - j\omega}$$

$$\text{so} \quad I(s) = \frac{\tilde{A}}{L} \frac{1}{(s - j\omega)(s + R/L)}$$

Question 4

①

$$a) X(s) = \frac{s}{s^2 + 100} - \frac{4}{s(s+2)} + 7.$$

$$\begin{aligned} x(t) &= \cos(10t) - 4 \int_0^t e^{-2z} dz + 7\delta(t) \\ &= \cos(10t) + 2e^{-2t} - 2 + 7\delta(t) \end{aligned}$$

$$b) L = 2 \text{ mH} \quad C = 15 \mu\text{F}$$

$$\alpha = \frac{R}{2L} \quad \beta = \frac{1}{LC} = \frac{1}{(2 \times 10^{-3}) \times (15 \times 10^{-6})} = 3.333 \times 10^7$$

for underdamped.

$$\alpha^2 < \beta \quad \text{or} \quad \frac{R^2}{4L^2} < \frac{1}{LC}$$


$$R^2 < \frac{4L}{C}$$

$$R < 2\sqrt{\frac{L}{C}} = 2\left(\frac{2 \times 10^{-3}}{15 \times 10^{-6}}\right)^{1/2} = 23.1 \Omega$$

②

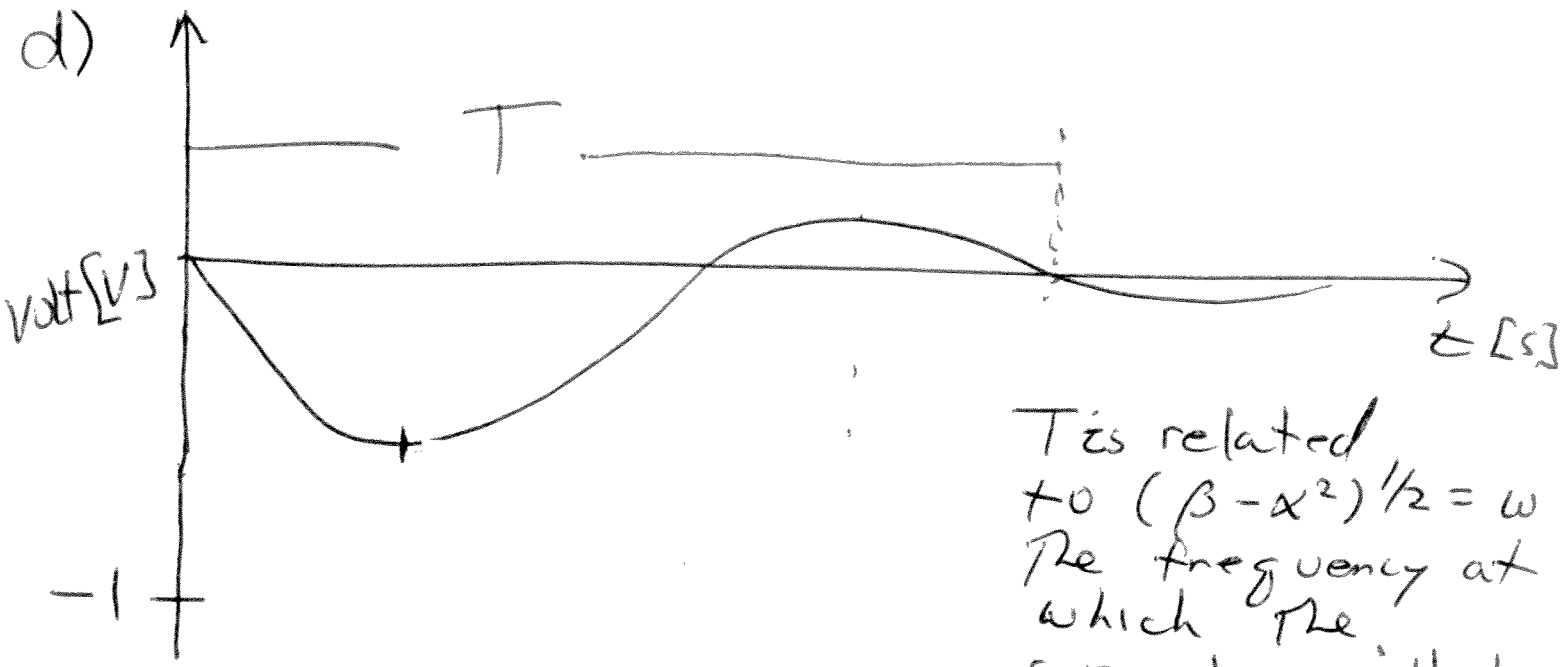c) for $x(t) = u(t-2) + 4\sin(\omega t) - 8t$

$$X(s) = \frac{e^{-2s}}{s} + \frac{4\omega}{s^2 + \omega^2} - \frac{8}{s^2}$$



T is related to $(\beta - \alpha^2)^{1/2} = \omega$ the frequency at which the circuit oscillates.

e) $\ddot{q} + 2\alpha\dot{q} + \beta q = v(t)$ for the charge on capacitor.

$$L \frac{di}{dt} + iR + \frac{q(0)}{C} + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

for the current.

$i(t) = \dot{q}(t)$ for the current.

$v_{RC}(t) = iR + q/C$ for the voltage drop across components.